

A High Efficiency Synchronous Buck VRM with Current Source Gate Driver

Wilson Eberle

Zhiliang Zhang

Dr. Yan-Fei Liu

Dr. P.C. Sen

Outline

1. Introduction

1. Why you should use current source gate drive
2. Drawbacks of existing voltage source and resonant based drivers

2. Proposed Driver and Operation

3. Driver Design Procedure

4. Driver Optimization in the VRM


5. Logic and Level Shift Circuits

6. Experimental Results

 7. Conclusions

Introduction

- **Application:** low voltage high current voltage regulator modules




Topology of Choice

Synchronous Buck

- Trend to increase switching frequency for improvements in:
 - + **power density**
 - + **dynamic performance**

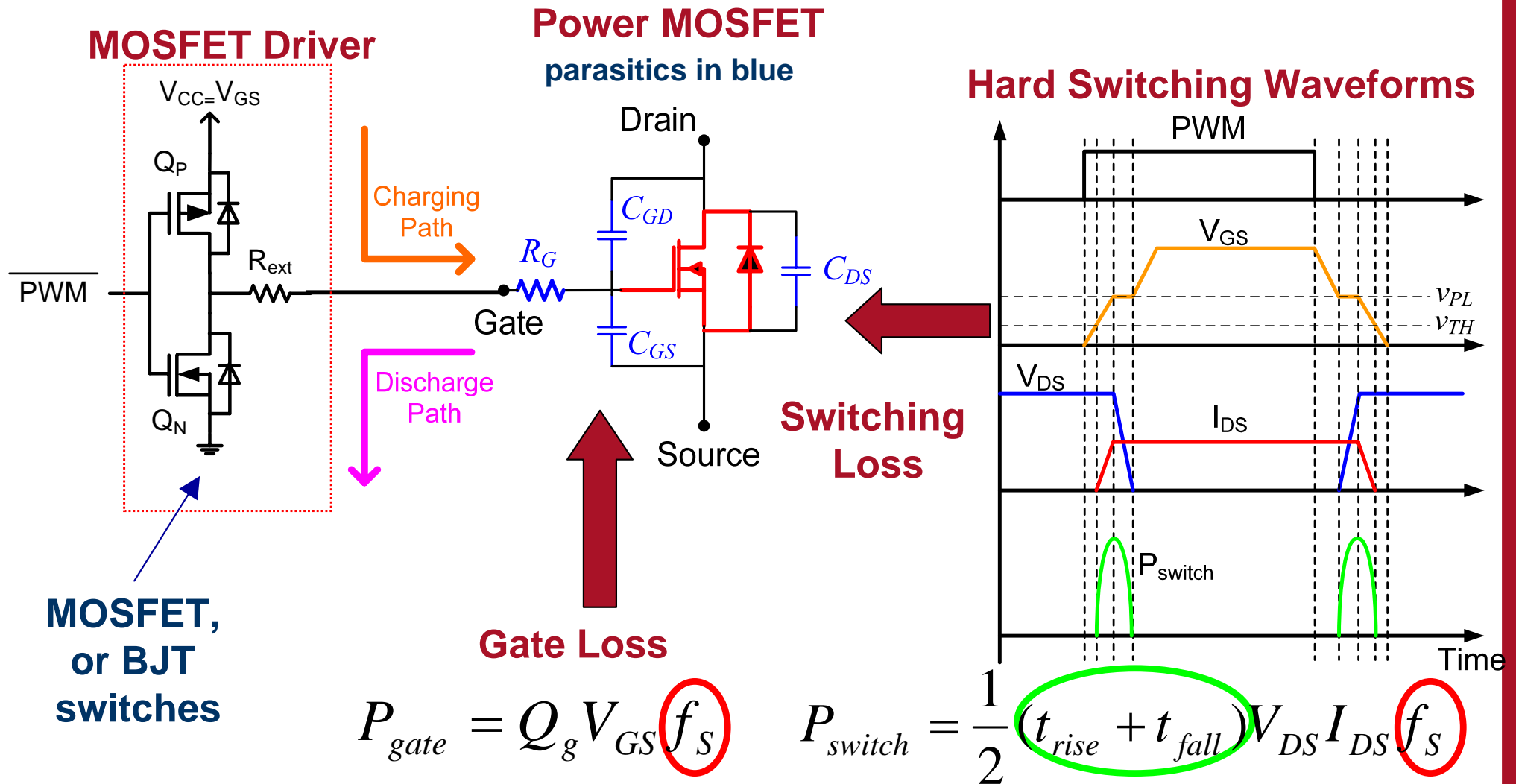Drawbacks of Increased Switching Frequency with Conventional Drivers





Resonant Gate Drive Techniques

- + Many good (~10) circuits proposed since early 1990s, but generally unused
- LC resonant charging of the power MOSFET gate from zero initial current
- These circuits emphasize gate energy savings, but ignore, or can't achieve potential switching loss savings

Resonant Gate Drive Review



Existing techniques suffer from at least one of five problems:

  1. Circulating current conduction loss
2. Peak current dependent on duty cycle




Resonant Gate Drive Review

  3. Large inductance, bulky transformer, or coupled inductor
4. Slow turn-on and/or turn-off
5. Gate not actively clamped high and/or low, so false triggering (Cdv/dt) can result



 Conventional vs. Resonant Drive Switching Loss Savings



**Voltage source
RC-type charging
limits speed**


**Constant current source
type charging
improves speed!**

**CURRENT SOURCE DRIVERS CAN
REDUCE TURN-ON AND TURN-OFF LOSS!**

Outline


1. Introduction
2. **Proposed Driver and Operation**
3. Driver Design Procedure
4. Driver Optimization in the VRM
5. Logic and Level Shift Circuits
6. Experimental Results
7. Conclusions

Proposed Driver

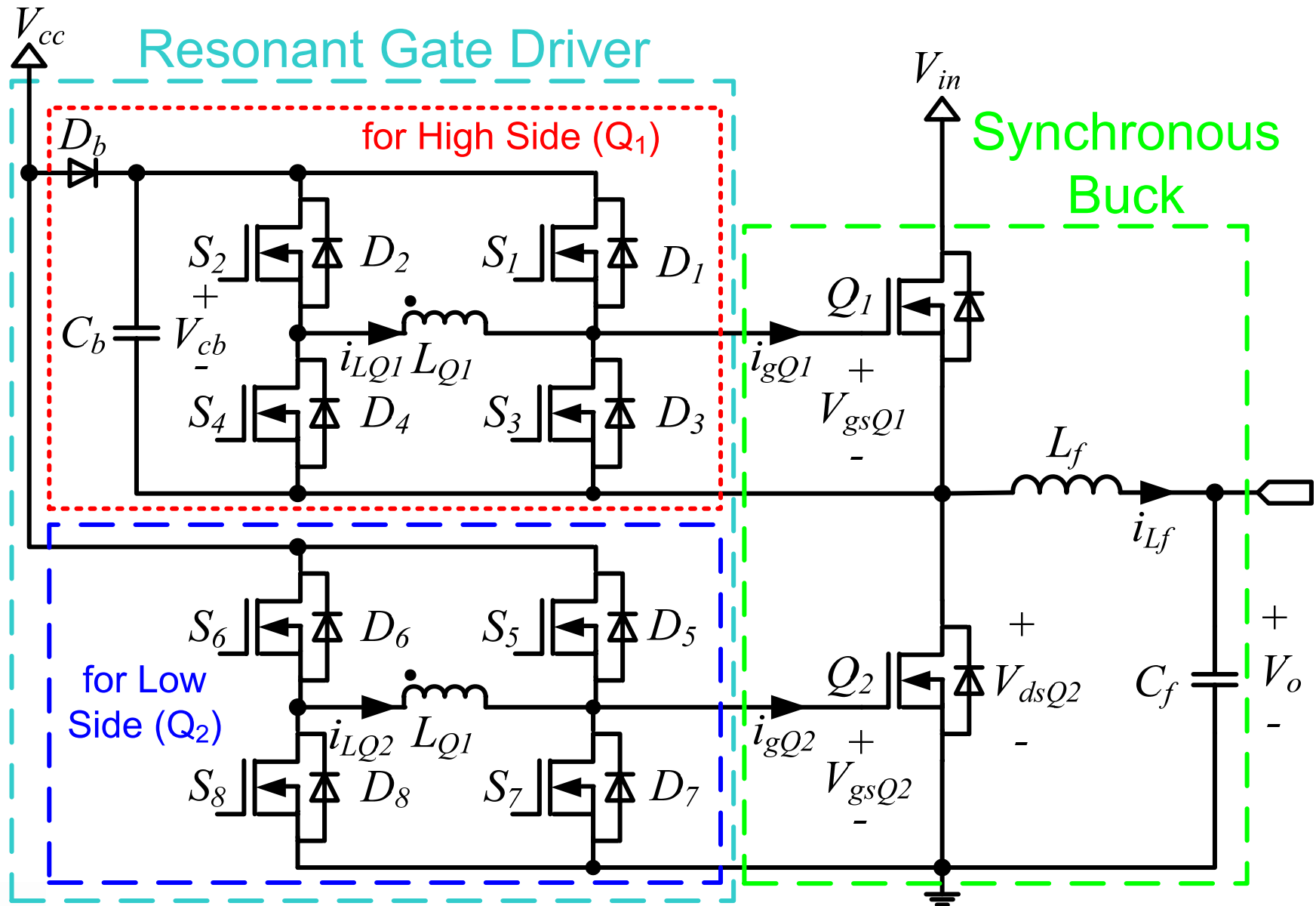


Creating a Discontinuous Current Source

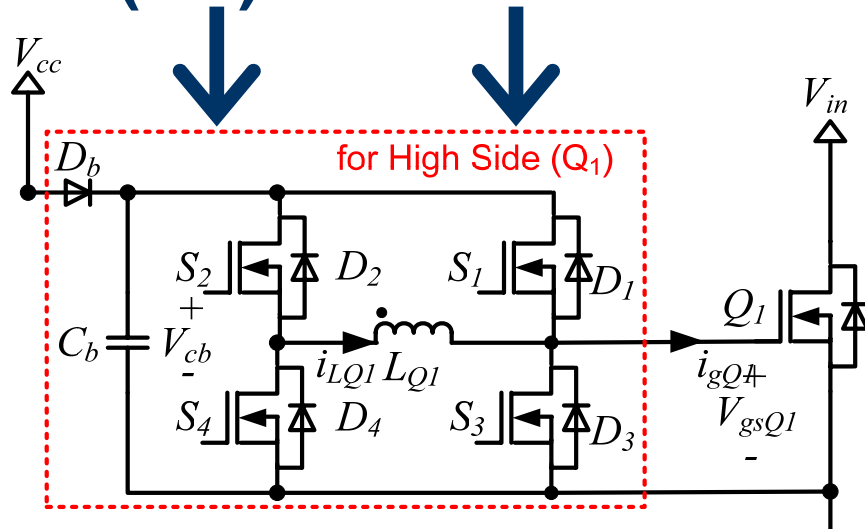Independent control of high side (HS) MOSFET and SR




Key To Speed:


 
- Create discontinuous inductor current source, then
- Divert inductor pre-charge current to the gate




High Side MOSFET Turn On Sequence

 

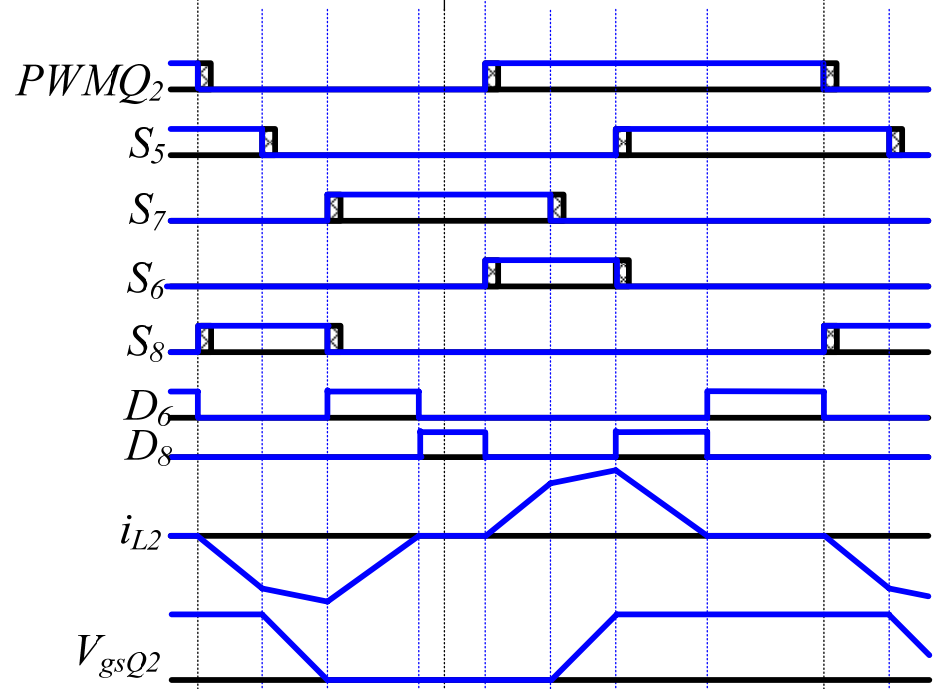
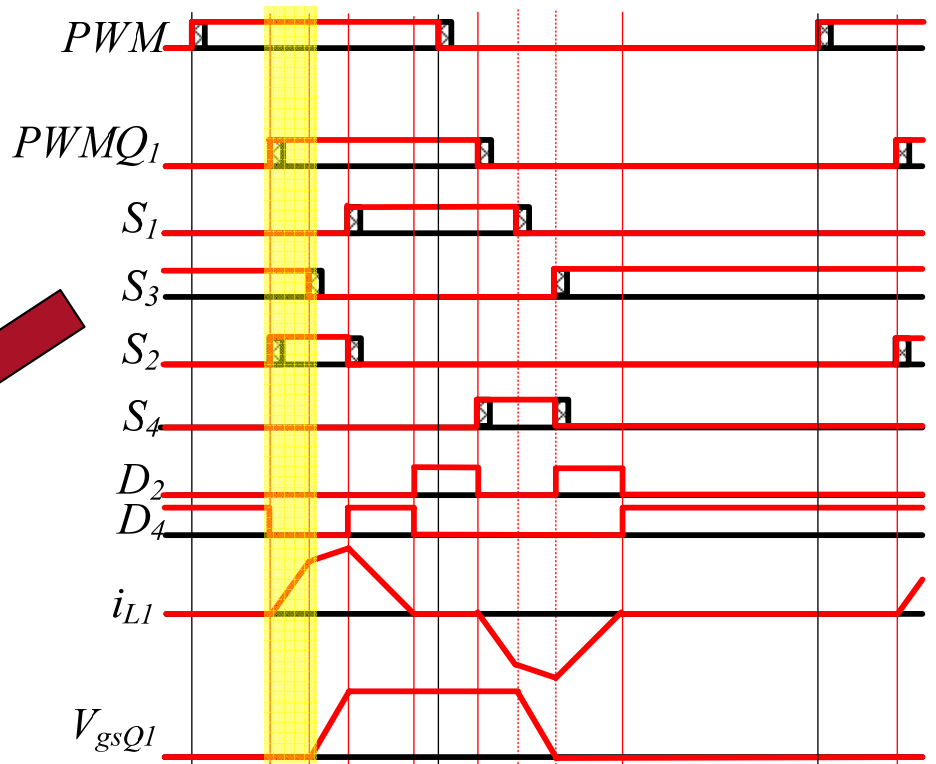
- Dictated by PWMQ₁ signal
- Independent control of HS MOSFET and SR




High Side MOSFET Turn On Sequence

 

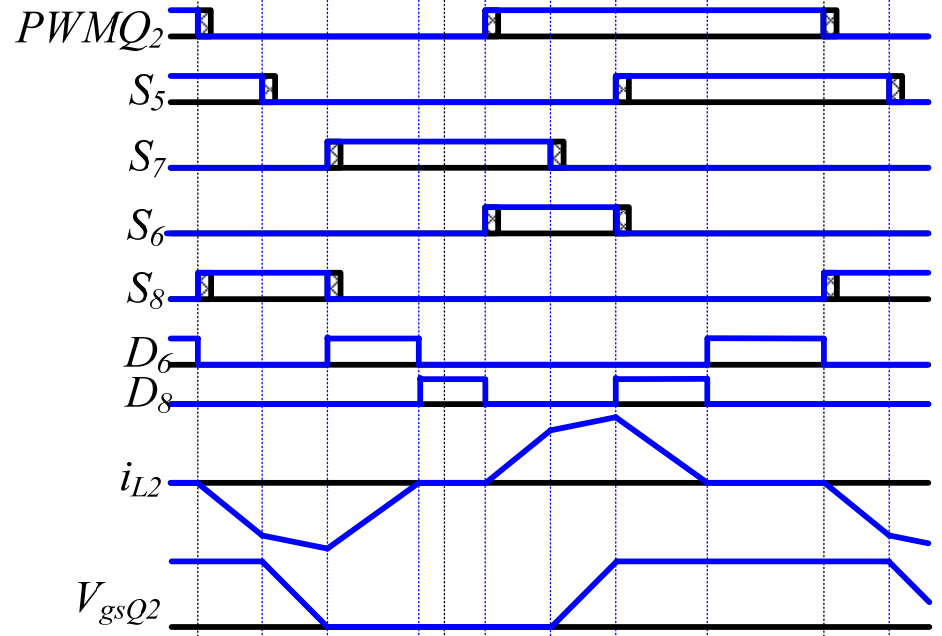
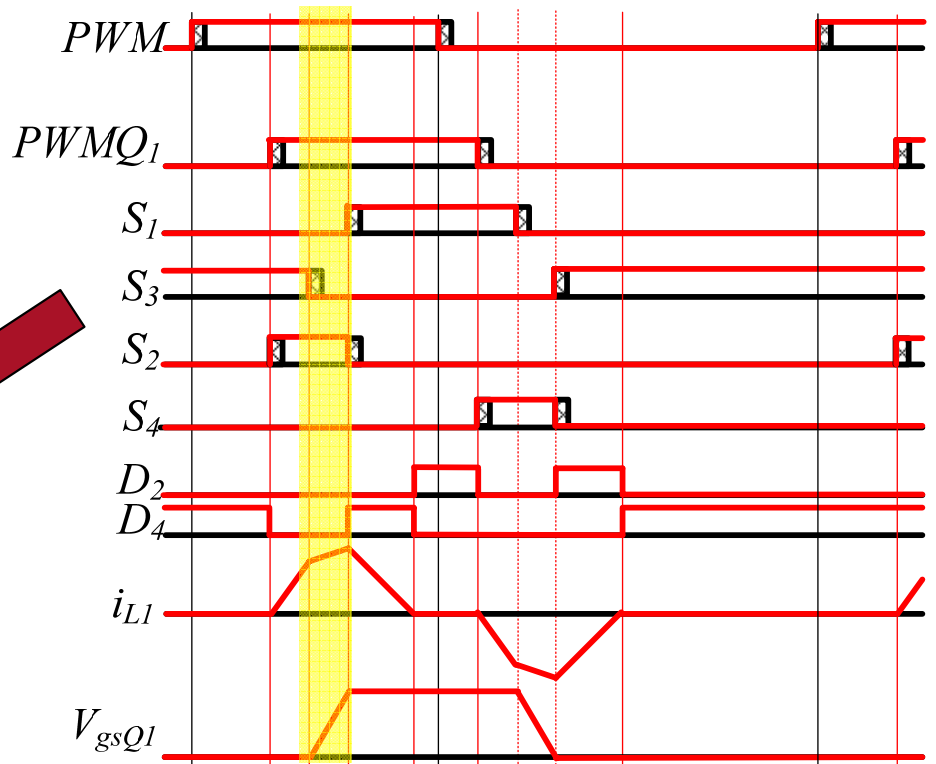
- Dictated by PWMQ₁ signal
- Independent control of HS MOSFET and SR




High Side MOSFET Turn On Sequence

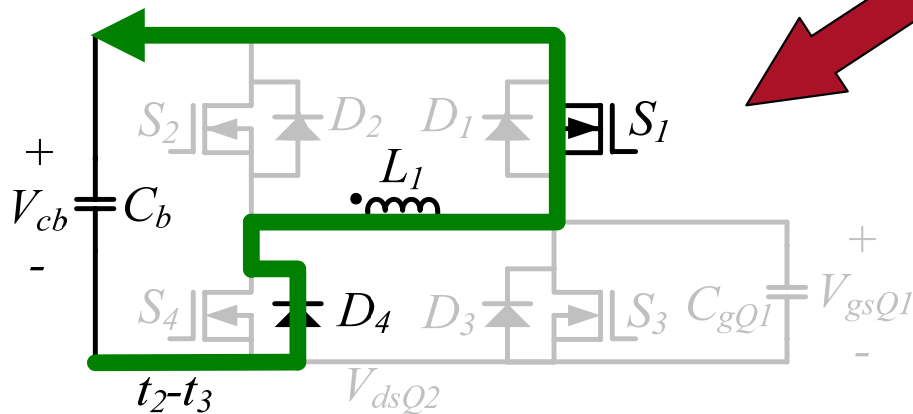

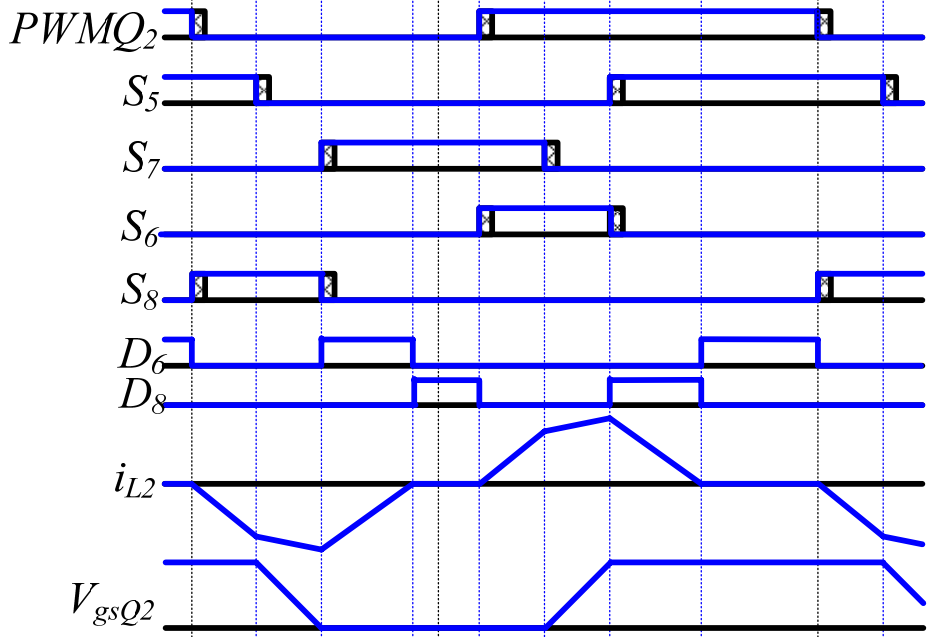 
- Dictated by $PWMQ_1$ signal
- Independent control of HS MOSFET and SR




High Side MOSFET Turn On Sequence

 

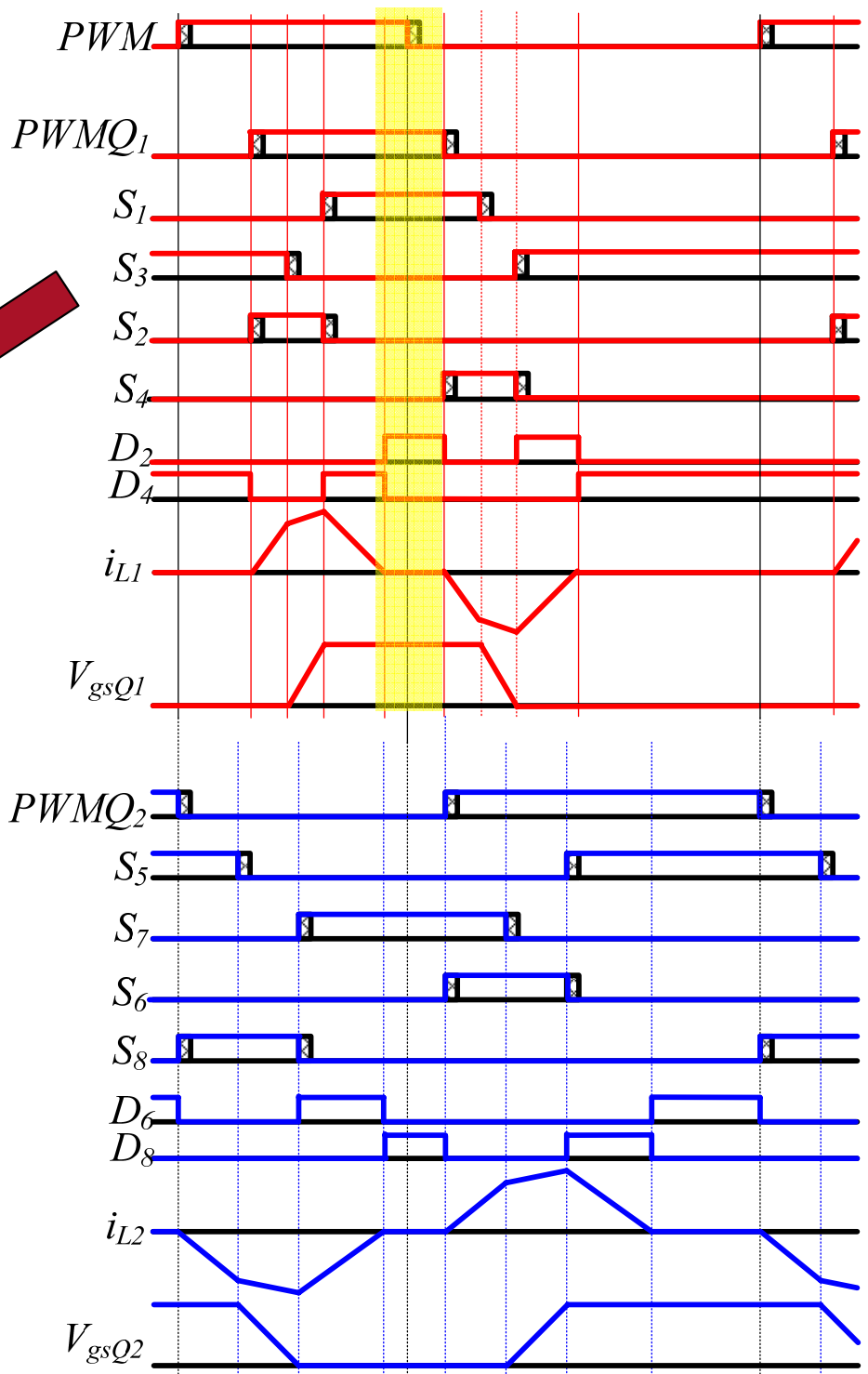
- Dictated by $PWMQ_1$ signal
- Independent control of HS MOSFET and SR



High Side MOSFET Turn Off Sequence


 


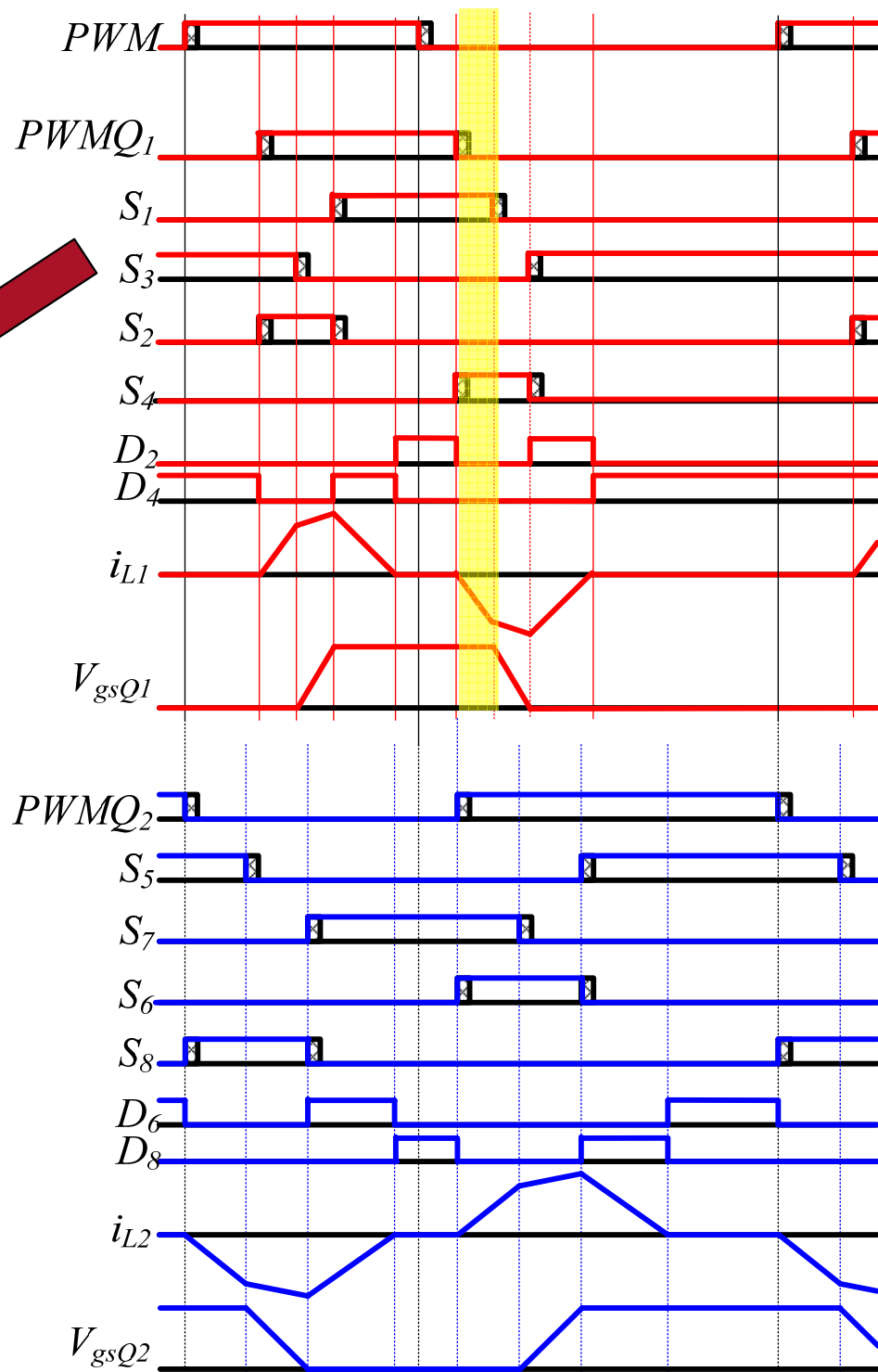- Dictated by $PWMQ_1$ signal
- Independent control of HS MOSFET and SR



SR Operation

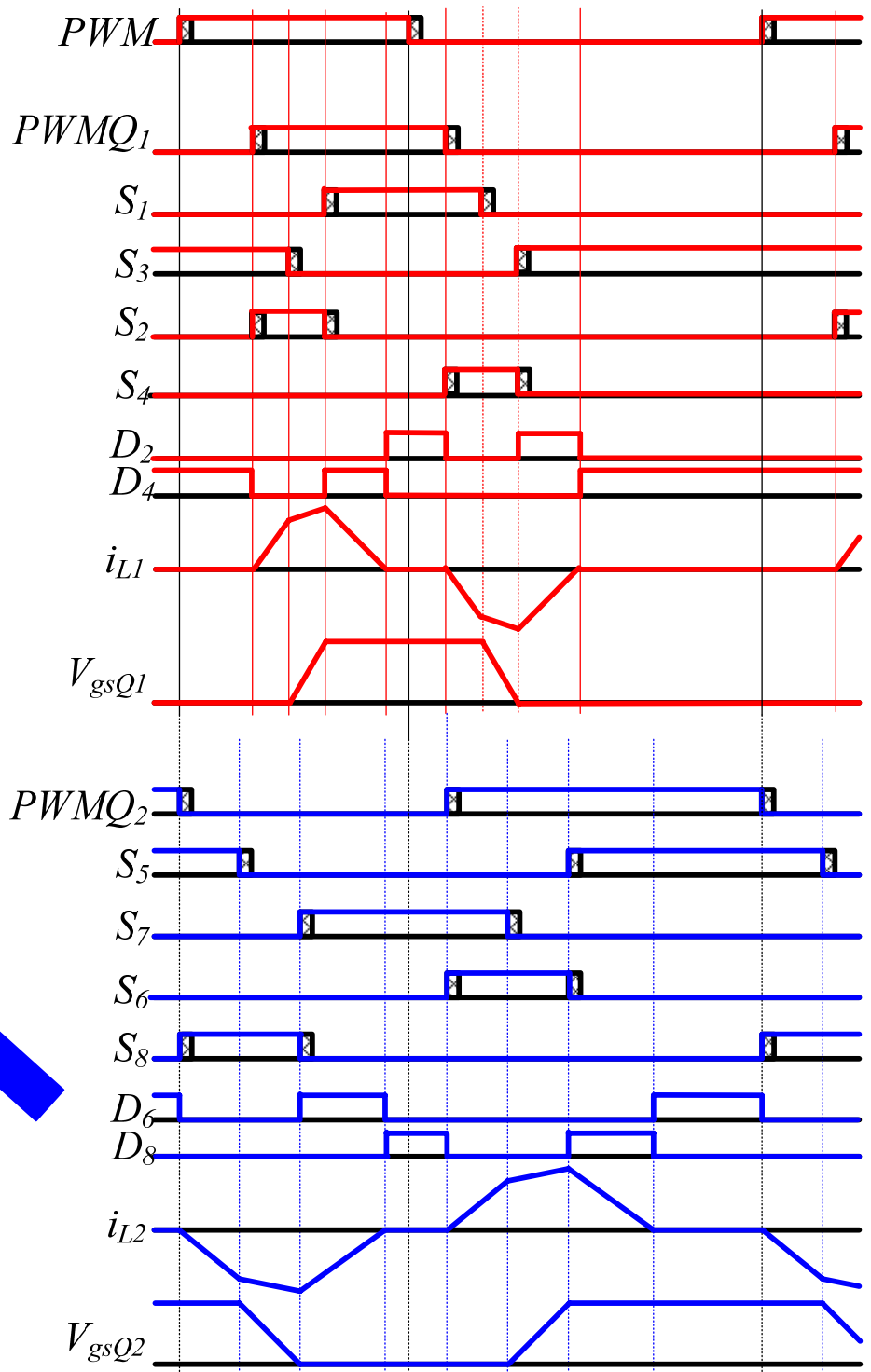 - Same procedure for SR
- Different time intervals due to larger gate charge
- Dictated by $PWMQ_2$ signal



Outline

1. Introduction
2. Proposed Driver and Operation
3. **Driver Design Procedure**
4. Driver Optimization in the VRM
5. Logic and Level Shift Circuits
6. Experimental Results
7. Conclusions


Driver Design

1. Set the turn on time, or average gate current
2. Set inductor pre-charge time
3. Calculate the inductor value

$$t_{on} = \frac{Q_g}{I_{g_{avg}}}, I_{g_{avg}} = \frac{Q_g}{t_{on}}$$

$$t_{d1} \approx \frac{1}{2} t_{on}$$

 
$$L_1 = \frac{V_{cb} t_{on}}{Q_g} \left(\frac{t_{on}}{4} + t_{d1} \right)$$




Outline

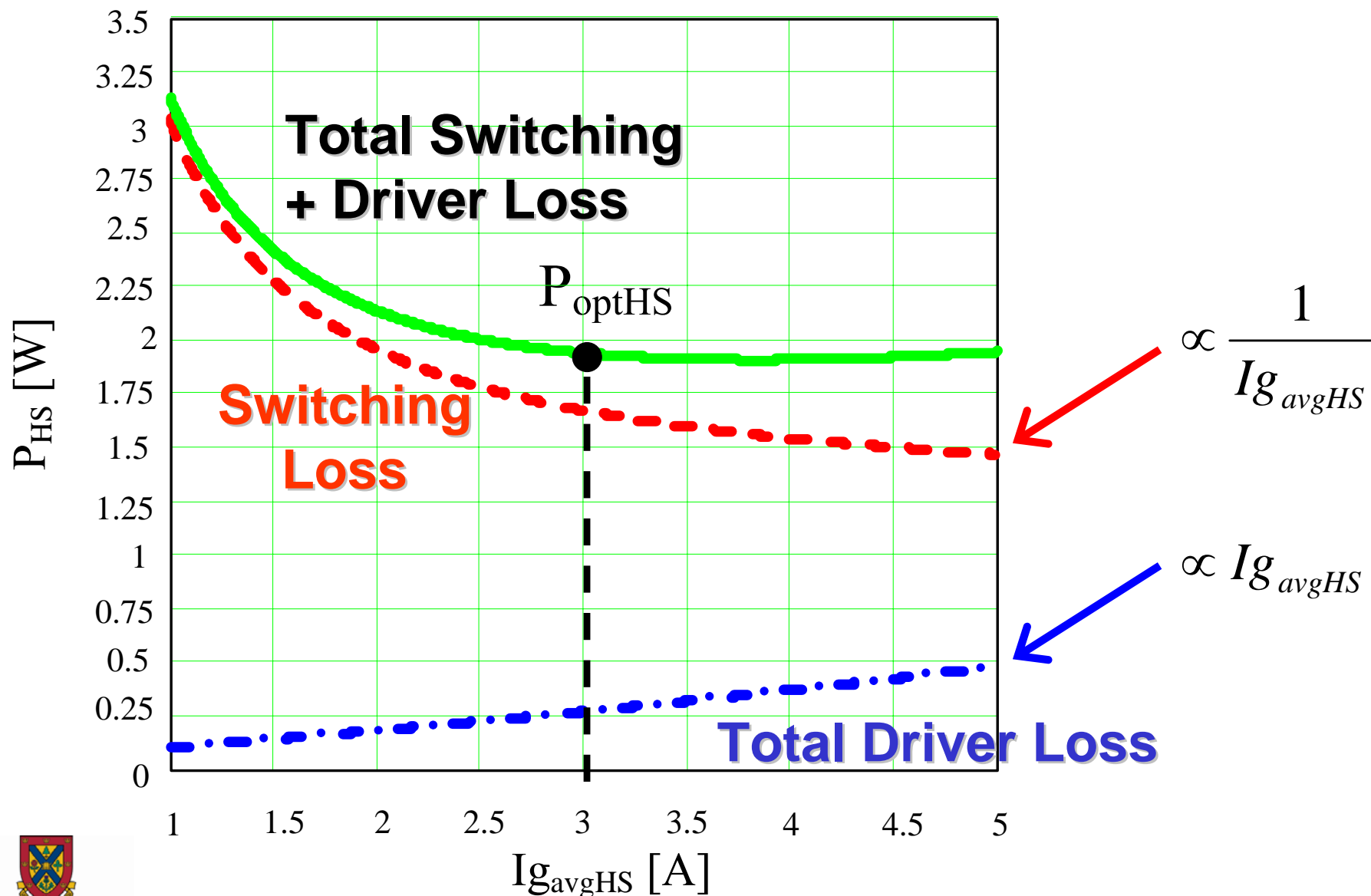1. Introduction
2. Proposed Driver and Operation
3. Driver Design Procedure
4. **Driver Optimization in the VRM**
5. Logic and Level Shift Circuits
6. Experimental Results
7. Conclusions

Optimizing HS Gate Current w.r.t. Driver Loss and Switching Loss






 
Optimizing SR Gate Current w.r.t. Driver Loss and Body Diode Loss



Outline

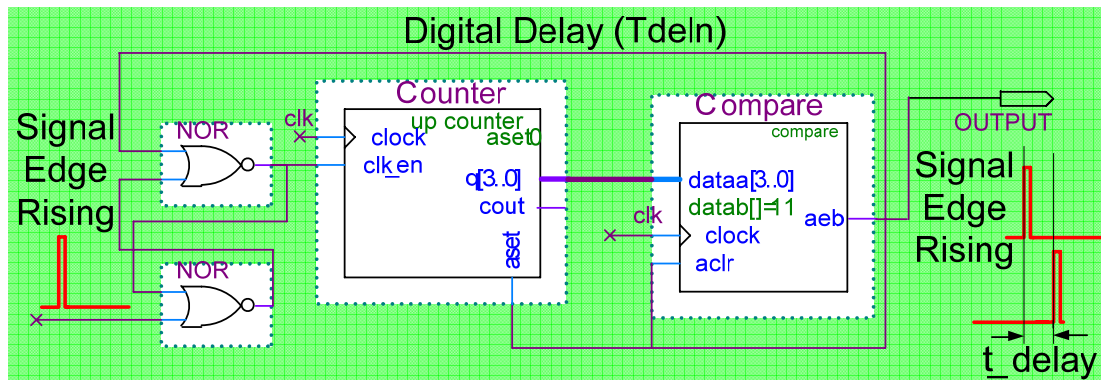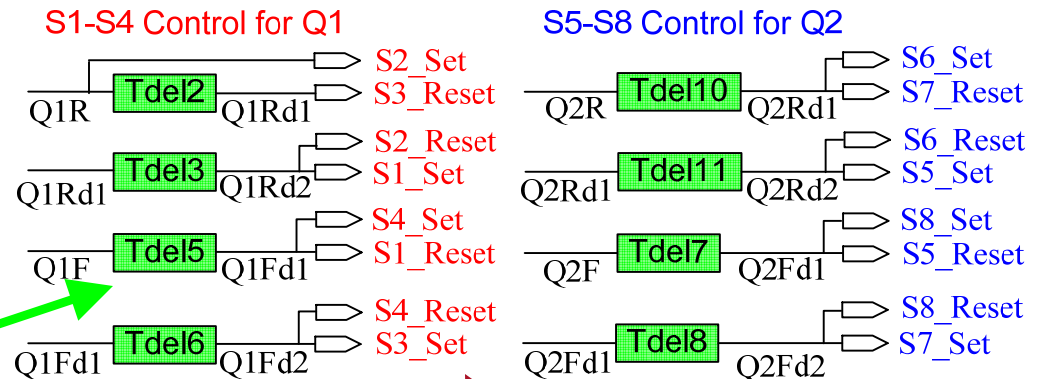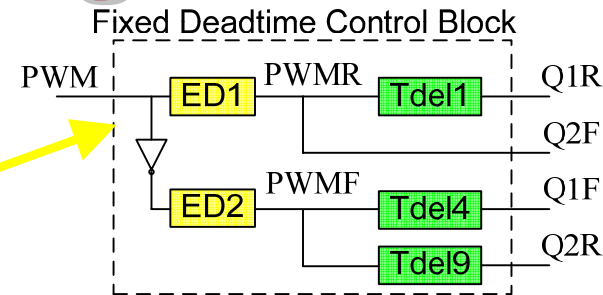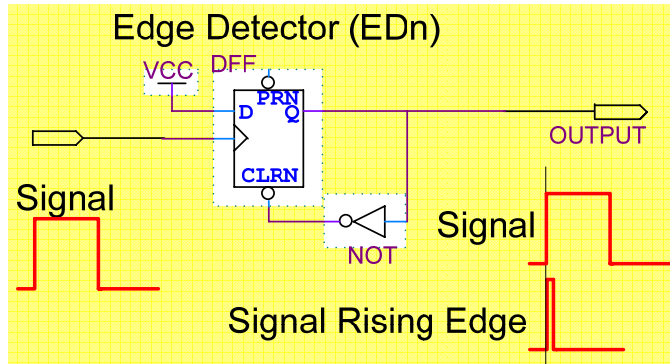1. Introduction
2. Proposed Driver and Operation
3. Driver Design Procedure
4. Driver Optimization in the VRM
5. Logic and Level Shift Circuits
6. Experimental Results
7. Conclusions

Logic Generation for Deadtime and S_1 - S_4 Gating Signals





HS
MOSFET

SR

Gating Signal
Outputs

Level Shift Circuit

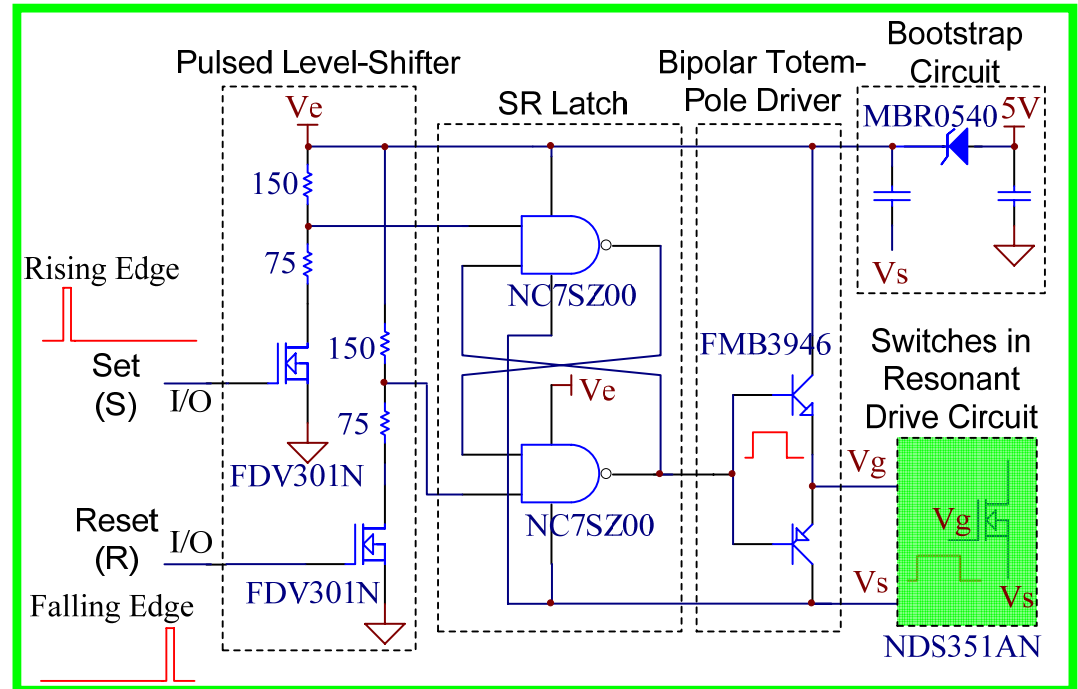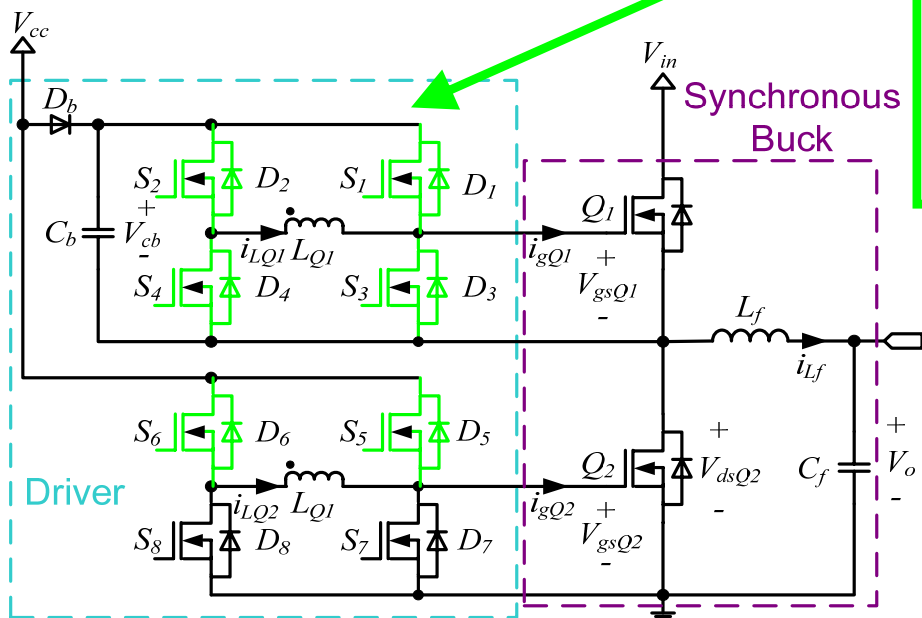6 Switches (S_1 - S_6)
Require
Level Shift
Circuits



Outline


1. Introduction
2. Proposed Driver and Operation
3. Driver Design Procedure
4. Driver Optimization in the VRM
5. Logic and Level Shift Circuits
6. Experimental Results
7. Conclusions

Experimental Setup and Specs

- **Single Phase Apples to apples comparison**
- 6-layer, 2oz
- 12V Input
- 1.3V Output
- Up to 30A Load
- **1MHz**
- IRF6617 HS
- IRF6691 SR
- 330nH inductor:
Vishay IHLP5050FD


Current Source Driver

 S_1 - S_8 : NDS351AN, L_1 : 68nH, L_2 : 307nH
2.5ns fixed maximum deadtime



Conventional Driver


UCC27222, Predictive deadtime control

 

Waveforms


**HS MOSFET
and SR
gate-source
waveforms**

 **HS MOSFET
Driver
Inductor
Current
Waveform**




Efficiency vs. Load

1MHz, 12V input, 1.3V load, 10V V_{cc}

 

Power Loss vs. Load


1MHz, 12V input, 1.3V load, 10V V_{cc}

 

 **2.5W
Improvement
Per
Phase!**

Implications of Loss Savings

- 15W savings (2.5Wx6) in a 6 phase VRM, or
- 120A output, assuming loss limited to 9W per phase:
 - **5 phases** required for conventional driver (27A max per phase; $120\text{A}/27\text{A}=5$ phases)
 - **4 phases** required for current source driver (30A max per phase; $120\text{A}/30\text{A}=4$ phases)
- **1 phase eliminated: A SIGNIFICANT COST SAVINGS**



Outline

1. Introduction
2. Proposed Driver and Operation
3. Driver Design Procedure
4. Driver Optimization in the VRM
5. Logic and Level Shift Circuits
6. Experimental Results
7. Conclusions

Summary of Advantages

- **Current source drive to increase switching speed, decrease switching loss and decrease conduction loss**
- **SR gate energy recovery (~50%) or higher operating V_{cc}**
- **Small driver inductors:**
 - **HS MOSFET: <100nH compared to 1uH+ for other competitor current source gate driver**
- **Optimized independent control of HS and SR gate currents**
- **Potential driver integration with no additional pins for HS MOSFET and 1 additional pin for SR**

Conclusions

- **Novel current source gate driver for synchronous buck VRM proposed**
- **Driver operation, design, optimization, logic, level shift and experimental results presented**
- **Driver achieves 4% efficiency improvement and 2.5W savings over conventional at 1MHz**
- **Elimination of 1 phase at 1.3V/120A load**

Acknowledgements

The authors would like to thank:

Ontario Centres of Excellence



C&D Technologies



Other interesting material available at:

www.queenspowergroup.com

Questions?